 


Implement the synchronous circuit
with the following state diagram

- Verilog + UWW simulation (50%) or
Verilog + testbench simulation (60%)
- FPGA (40%)

Simulation must
have at least 10
state transitions



- You must output the state in both
simulation and FPGA